

Total No. of Printed Pages—6

## 3 SEM TDC PHYH (CBCS) C 7

**2 0 2 1**

( Held in January/February, 2022 )



### PHYSICS

( Core )

Paper : C-7

( Digital Systems and Applications )

*Full Marks : 53*  
*Pass Marks : 21*

*Time : 3 hours*

*The figures in the margin indicate full marks  
for the questions*

1. Choose the correct option :  $1 \times 5 = 5$

- (a) In a CRT, the focus can be controlled by
- (i) adjusting the positive potential of the anode
  - (ii) adjusting the negative potential of the grid
  - (iii) adjusting the d.c. potential of the horizontal deflection plates
  - (iv) adjusting the d.c. potential of the vertical deflection plates

( 2 )

(b) The binary equivalent of the decimal number 52.875 is

(i) 100110.101

(ii) 100100.110

(iii) 110100.111

(iv) 111010.011

(c) The maxterm which is missing in the expression  $A(\bar{B} + A)B$  is

(i)  $M_0$

(ii)  $M_1$

(iii)  $M_2$

(iv)  $M_3$

(d) Which of the following is **not** correct?

(i)  $\overline{A \oplus B} = \bar{A} \oplus B$

(ii)  $A \oplus B = \bar{A} \oplus \bar{B}$

(iii)  $A + BC = (A + B)(A + C)$

(iv)  $A \oplus \bar{A} = 0$

( 3 )

(e) When a flip-flop is reset, its outputs will be

(i)  $Q = 0, \bar{Q} = 0$

(ii)  $Q = 1, \bar{Q} = 0$

(iii)  $Q = 0, \bar{Q} = 1$

(iv)  $Q = 1, \bar{Q} = 1$

2. Draw the block diagram of a general purpose CRO and mention the different parts.

2

3. What are different scales of integration? Mention the number of components in each scale of integration.

2

4. (a) Describe how NAND gate can be used to realize XOR gate.

3

(b) Draw the logic diagram and write the truth table of an even parity bit generator using XOR gate (consider 4-bit input).

2

22P/96

( Turn Over )


ND

Dr RAMA VERMA

( 4 )

5. Draw the simplest possible logic diagram that implements the output of the logic diagram shown below :

3

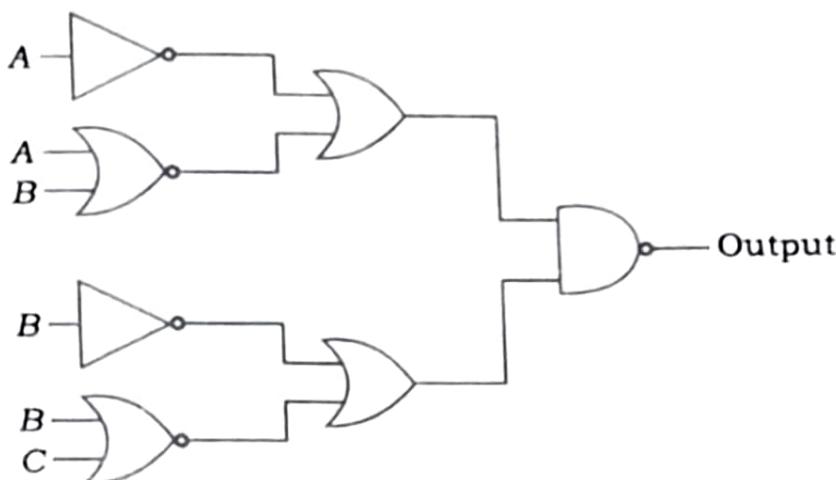

Or

Reduce the expression  $f = \Sigma m(0, 2, 3, 4, 5, 6)$   
using K-map and implement it using AOI  
logic.

2+1=3

6. Draw the logic diagram of a decimal to BCD encoder and explain its working.

2+2=4

7. (a) Describe the 2's complement method of subtraction.  
(b) What is half adder? Draw the logic diagram for half adder using only NAND gates.

2

1+2=3

12.

A  
( 5 )

8. How does a *J-K* flip-flop differ from an *S-R* flip-flop in its operation? Draw the logic diagram of an active-high *S-R* latch using only *NAND* gates and describe its operation.

1+3=4

*Or*

- What is race around condition in flip-flop?  
Explain how master-slave flip-flops can  
eliminate this condition.

1+3=4

9. Draw the functional block diagram of an IC-555 and explain the function of each pin. 3

10. Draw the logic diagram of 4-bit serial-in, parallel-out shift register using *D* flip-flops. 2

11. What is ring counter? Describe the working of a 4-bit ring counter. 1+3=4

*Or*

- What is synchronous counter? Describe the procedure for systematic design of any synchronous counter. 1+3=4

12. (a) What are different types of secondary memory? Write one advantage of DDR RAM. 1+1=2

- (b) Explain the functions of different buses present in a computer. 3

- 13.** (a) What are the various registers of 8085 microprocessor? 2  
 (b) Describe the different types of addressing modes of 8085 microprocessor. 4

*Or*

Draw the simplified block diagram of 8085 microprocessor showing the main units. 4

- 14.** Define opcode and operant. Explain the arithmetic instruction of 8085 with example.

$$1+2=3$$

★ ★ ★

